

$$P_{out} := 200 \text{ mW} \quad R_{load} := 16 \text{ } \Omega \quad R_{in_min} := 10 \text{ k}\Omega \quad R_{out_max} := 5 \text{ } \Omega$$

$$BW_{min} := 20 \text{ kHz} \quad V_{in} := 20 \text{ mV} \quad \text{amplitude}$$

$$V_{out} := \sqrt{P_{out} \cdot R_{load}} = 1.789 \text{ V}$$

$$V_T := 25 \text{ mV}$$

$$I_{out} := \sqrt{\frac{P_{out}}{R_{load}}} = 111.803 \text{ mA}$$

$$A_{CE} := 3$$

$$\frac{V_{out}}{\frac{V_{in}}{\sqrt{2}}} = 126.491$$

$$A_{diff} := 42$$

$$\beta_{AB} := 90$$

$$\beta := 325$$

$$V_{CC} := 15 \text{ V} \quad V_{EE} := -15 \text{ V}$$

$$f_c := 20 \text{ kHz}$$

$$X_C = \frac{1}{2 \pi \cdot f \cdot C}$$

$$C := 470 \text{ } \mu\text{F}$$

$$\frac{1}{2 \pi \cdot f_c \cdot C} = 0.017 \text{ } \Omega$$

Class AB

$$V_{BN} := 0.7 \text{ V} \quad V_{BP} := -0.7 \text{ V}$$

$$A_{AB} := 1.5$$

$$V_{BB} := V_{BN} - V_{BP} = 1.4 \text{ V}$$

$$i_{L_max} := \sqrt{\frac{P_{out}}{R_{load}}} = 111.803 \text{ mA}$$

$$V_{BEQ1} := 0.7 \text{ V}$$

$$fA := 10^{-15} \text{ A}$$

$$i_{B_max_AB} := \frac{i_{L_max}}{\beta_{AB}} = 1.242 \text{ mA}$$

$$I_{bias} := 3 \text{ mA}$$

$$\frac{V_T}{\frac{i_{L_max}}{2}} = 0.447 \text{ } \Omega$$

$$I_R := 1 \text{ mA}$$

$$I_{C1} := I_{bias} - I_R = 2 \text{ mA}$$

$$I_S := \frac{I_{C1}}{\frac{V_{BB}}{2 \cdot V_T} e} = 1.383 \text{ fA}$$

$$R_{eq} := \frac{V_{BB}}{I_R} = 1.4 \text{ k}\Omega$$

$$R_1 := \frac{V_{BEQ1}}{I_R} = 700 \text{ } \Omega$$

$$R_2 := R_{eq} - R_1 = 700 \text{ } \Omega$$

$$V_{CC} = 15 \text{ V}$$

Constant current source Zener diode


$$V_{zener} := 13 \text{ V} \quad V_{diode} := 0.7 \text{ V}$$

$$V_{Eset} := V_{CC} - V_{zener} + V_{diode} = 2.7 \text{ V}$$

$$R_{set} := \frac{V_{CC} - V_{Eset}}{I_{bias}} = 4.1 \text{ k}\Omega$$

$$I_{zener} := 5 \text{ mA}$$
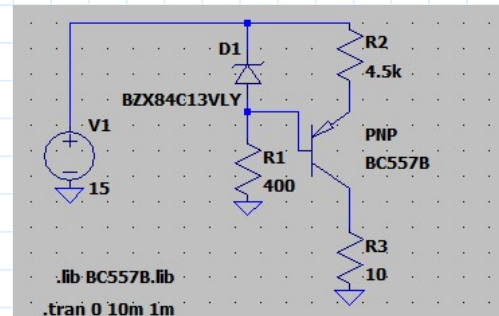
$$R_Z := \frac{V_{CC} - V_{zener}}{I_{zener}} = 400 \text{ } \Omega$$



Output modstand

$$V_B := 1.4 \text{ V} \quad V_{BE} := 0.7 \text{ V}$$

$$V_E := V_B - V_{BE} = 0.7 \text{ V}$$

$$I_E := \frac{V_E}{R_{load}} = 43.75 \text{ mA}$$

$$R_{out} := \frac{V_T}{I_E} = 0.571 \text{ }\Omega$$

WAS trin

$$i_{C_max_WAS} := i_{B_max_AB} = 1.242 \text{ mA}$$

$$A_{CE} = 3$$

$$R_{IN} = (\beta + 1) \cdot (r_e \cdot R_E)$$

$$i_B = \frac{v_{in}}{R_{IN}}$$

$$v_o = -R_C \cdot i_b \cdot \beta$$

$$v_o = -R_C \cdot \frac{v_i}{R_{IN}} \cdot \beta$$

$$\frac{v_o}{v_i} = -\frac{R_C}{(r_e + R_E)} \cdot \frac{\beta}{\beta + 1}$$

$$\frac{v_o}{v_i} = -\alpha \cdot \frac{R_C}{r_e + R_E} = -\alpha \frac{R_C}{R_E} \quad \alpha := \frac{\beta}{\beta + 1} = 0.997$$

$$R_C := 4.7 \text{ k}\Omega$$

$$A_{CE} = -\alpha \cdot \frac{R_C}{R_E} \quad R_E := \alpha \cdot \frac{R_C}{A_{CE}} = 1.562 \text{ k}\Omega$$

DC

$$V_B = \frac{R_{B1} + R_{B2}}{R_{B1} \cdot R_{B2}} \cdot V_{CC} \quad V_{CE} := 4 \text{ V} \quad V_{RC} := 13 \text{ V} \quad V_C := 2 \text{ V}$$

$$V_E := -2 \text{ V} \quad V_{RE} := V_E - V_{EE} = 13 \text{ V}$$

$$V_B := V_E + V_{BE} = -1.3 \text{ V}$$

$$R_{B1} := 5.1 \text{ k}\Omega$$

$$V_B = \frac{R_{B1} - R_{B2}}{R_{B1} + R_{B2}} \cdot V_{CC} \xrightarrow{\text{solve, } R_{B2}} \frac{-5.1 \cdot \text{k}\Omega \cdot V - 58.846153846153846154 \cdot \text{k}\Omega \cdot V}{V - 11.538461538461538462 \cdot V}$$

$$R_{B2} := \frac{-5.1 \cdot \text{k}\Omega \cdot V - 58.846153846153846154 \cdot \text{k}\Omega \cdot V}{V - 11.538461538461538462 \cdot V} = 6.068 \text{ k}\Omega$$

$$I_E := \frac{V_E - V_{EE}}{R_E} = 8.323 \text{ mA}$$

$$I_B := \frac{I_E}{(\beta + 1)} = 25.532 \text{ }\mu\text{A} \quad \text{S.429}$$

Commen mode amplifier

DC analyse

$$V_{C_CM} := V_B = -1.3 \text{ V} \quad I_{EE_CM} := 4 \text{ mA} \quad \alpha = 0.997$$

$$I_{E_CM} := \frac{I_{EE_CM}}{2} = 2 \text{ mA}$$

$$V_{C_CM} = V_{CC} - R_{C_CM} \cdot I_{E_CM} \cdot \alpha$$

$$V_{BE} = 0.7 \text{ V}$$

$$R_{C_CM} := \frac{V_{CC} - V_{C_CM}}{I_{E_CM} \cdot \alpha} = 8.175 \text{ k}\Omega$$

$$0 \text{ V} + V_{BE} + I_{E_CM} \cdot R_{E_CM} + V_{ce} - V_{EE} = 0$$

AC

$$r_e := \frac{V_T}{I_{E_CM}} = 12.5 \text{ }\Omega \quad A_{diff} = 42$$

$$\frac{v_d}{2} = i_b \cdot r_\pi + i_e \cdot R_{E_CM} = i_b \cdot (\beta + 1) \cdot r_e + i_b \cdot (\beta + 1) \cdot R_{E_CM} = i_b \cdot (\beta + 1) (r_e + R_{E_CM})$$

$$v_d = 2 \cdot i_b \cdot (\beta + 1) (r_e + R_{E_CM})$$

$$v_{o1_cm} = -\beta \cdot i_{b_cm} \cdot R_{C_CM}$$

$$\frac{v_{o1_cm}}{v_d} = \frac{-\beta \cdot i_b \cdot R_{C_CM}}{2 \cdot i_b \cdot (\beta + 1) \cdot (r_e + R_{E_CM})} = -\frac{\beta \cdot R_{C_CM}}{2 \cdot (\beta + 1) \cdot (r_e + R_{E_CM})}$$

$$A_{diff} = \frac{\beta \cdot R_{C_CM}}{2 \cdot (\beta + 1) \cdot (r_e + R_{E_CM})} \xrightarrow{\text{solve}, R_{E_CM}} -12.5 \cdot \Omega + 0.097023809523809513402 \cdot \text{k}\Omega$$

$$R_{E_CM} := 12.5 \cdot \Omega + 0.097023809523809513402 \cdot \text{k}\Omega = 109.524 \text{ }\Omega$$

$$R_{IN} := 2 \cdot (\beta + 1) (r_e + R_{E_CM}) = 79.56 \text{ k}\Omega$$

$$V_{ce} := -V_{EE} - V_{BE} - I_{E_CM} \cdot R_{E_CM} = 14.081 \text{ V}$$

Strøm spejl

$$I_{C_SP} := I_{EE_CM} = 4 \text{ mA}$$

$$I_{B_SP} := \frac{I_{C_SP}}{\beta} = 12.308 \text{ }\mu\text{A}$$

$$I_{R_SP} := I_{B_SP} \cdot 2 + I_{C_SP} = 4.025 \text{ mA}$$

$$V_{CC} - R_{SP} \cdot I_{R_SP} - V_{BE} - V_{EE} = 0$$

$$R_{SP} := \frac{V_{CC} - V_{EE}}{I_{R_SP}} = 7.454 \text{ k}\Omega$$