

$$P_{out} := 200 \text{ mW} \quad R_{load} := 16 \text{ } \Omega \quad R_{in_min} := 10 \text{ k}\Omega \quad R_{out_max} := 5 \text{ } \Omega$$

$$BW_{min} := 20 \text{ kHz} \quad V_{in} := 20 \text{ mV} \quad \text{amplitude}$$

$$V_{out} := \sqrt{P_{out} \cdot R_{load}} = 1.789 \text{ V}$$

$$V_T := 25 \text{ mV}$$

$$I_{out} := \sqrt{\frac{P_{out}}{R_{load}}} = 111.803 \text{ mA}$$

$$A_{CE} := 3$$

$$\frac{V_{out}}{\frac{V_{in}}{\sqrt{2}}} = 126.491$$

$$A_{diff} := 42$$

$$\beta_{AB} := 90$$

$$\beta := 325$$

$$V_{CC} := 15 \text{ V}$$

$$V_{EE} := -15 \text{ V}$$

$$\frac{I_{out}}{\beta_{AB}} = 1.242 \text{ mA}$$

$$f_c := 20 \text{ kHz}$$

Class AB

$$V_{BN} := 0.7 \text{ V} \quad V_{BP} := -0.7 \text{ V}$$

$$A_{AB} := 1.5$$

$$V_{BB} := V_{BN} - V_{BP} = 1.4 \text{ V}$$

$$i_{L_max} := \sqrt{\frac{P_{out}}{R_{load}}} = 111.803 \text{ mA}$$

$$V_{BEQ1} := 0.7 \text{ V}$$

$$fA := 10^{-15} \text{ A}$$

$$i_{B_max_AB} := \frac{i_{L_max}}{\beta_{AB}} = 1.242 \text{ mA}$$

$$I_{bias} := 3 \text{ mA}$$

$$\frac{V_T}{\frac{i_{L_max}}{2}} = 0.447 \text{ } \Omega$$

$$I_R := 1 \text{ mA}$$

$$I_{C1} := I_{bias} - I_R = 2 \text{ mA}$$

$$I_S := \frac{I_{C1}}{\frac{V_{BB}}{e^{2 \cdot V_T}}} = 1.383 \text{ fA}$$

$$R_{eq} := \frac{V_{BB}}{I_R} = 1.4 \text{ k}\Omega$$

$$R_1 := \frac{V_{BEQ1}}{I_R} = 700 \text{ } \Omega$$

$$R_2 := R_{eq} - R_1 = 700 \text{ } \Omega$$

$$V_{CC} = 15 \text{ V}$$

Constant current source Zener diode (bruges ikke)

$$V_{zener} := 13 \text{ V} \quad V_{diode} := 0.7 \text{ V}$$

$$V_{Eset} := V_{CC} - V_{zener} + V_{diode} = 2.7 \text{ V}$$


$$R_{set} := \frac{V_{CC} - V_{Eset}}{I_{bias}} = 4.1 \text{ k}\Omega$$

$$I_{zener} := 5 \text{ mA}$$

$$R_Z := \frac{V_{CC} - V_{zener}}{I_{zener}} = 400 \text{ } \Omega$$

$$V_{Cset} := V_{Eset} - 0.3 \text{ V} = 2.4 \text{ V}$$

$$V_{Cset} := V_{CC}$$

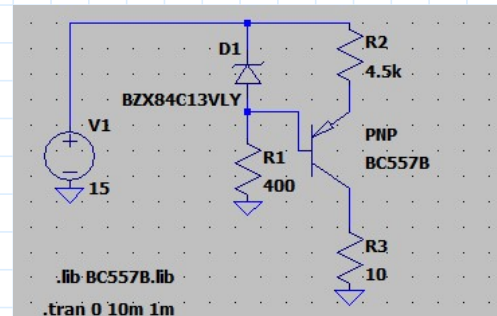

$$V_{B_AB1} := 0.6 \text{ V}$$

$$R_{1_AB} := \frac{V_{Cset} - V_{B_AB1}}{I_{bias}} = 4.8 \text{ k}\Omega$$

$$V_{B_AB1} := V_{Cset} - R_{1_AB} \cdot I_{bias} = 0.6 \text{ V}$$

$$V_{BE} := 0.7 \text{ V}$$

$$V_{B_AB2} := V_{B_AB1} - V_{BB} = -0.8 \text{ V}$$

$$R_{2_AB} := \frac{V_{B_AB2} - V_{EE} - V_{BE}}{I_{bias}} = 4.5 \text{ k}\Omega$$

Strøm spejl

$$I_{C_SP} := I_{bias} = 3 \text{ mA}$$

$$I_{B_SP} := \frac{I_{C_SP}}{\beta} = 9.231 \text{ }\mu\text{A}$$

$$I_{R_SP} := I_{B_SP} \cdot 2 + I_{C_SP} = 3.018 \text{ mA}$$

Output modstand

$$V_B := 1.4 \text{ V}$$

$$V_E := V_B - V_{BE} = 0.7 \text{ V}$$

$$I_E := \frac{V_E}{R_{load}} = 43.75 \text{ mA}$$

$$R_{out} := \frac{V_T}{I_E} = 0.571 \text{ }\Omega$$

$$V_{CC} - R_{SP} \cdot I_{R_SP} - V_{BE} - V_{EE} = 0$$

$$R_{SP} := \frac{V_{CC} - V_{EE} - V_{BE}}{I_{R_SP}} = 9.707 \text{ k}\Omega$$

$$R_{SP} := 10 \text{ k}\Omega$$

$$I_{R_SP} := \frac{V_{CC} - V_{EE} - V_{BE}}{R_{SP}} = 2.93 \text{ mA}$$

CC AMP

$$R_{E_CC} := 500 \text{ }\Omega$$

$$V_{E_CC} := V_{B_AB2} = -0.8 \text{ V}$$

$$\alpha := \frac{\beta}{\beta + 1} = 0.997$$

$$I_{E_CC} := \frac{V_{E_CC} - V_{EE}}{R_{E_CC}} = 28.4 \text{ mA}$$

$$I_{B_CC} := \frac{I_{E_CC}}{\beta + 1} = 87.117 \text{ }\mu\text{A}$$

$$I_{C_CC} := \alpha \cdot I_{E_CC} = 28.313 \text{ mA}$$

$$V_{B_CC} := V_{E_CC} + 0.7 \text{ V} = -0.1 \text{ V}$$

$$R_{B_CC} := \frac{V_{CC} - V_{B_CC}}{I_{B_CC}} = 173.331 \text{ k}\Omega$$

$$V_{CE_CC} := 0.5 \text{ V}$$

$$V_{C_CC} := V_{E_CC} + V_{CE_CC} = -0.3 \text{ V}$$

$$R_{C_CC} := \frac{V_{CC} - V_{C_CC}}{I_{C_CC}} = 540.39 \text{ }\Omega$$

WAS trin

$$i_{C_max_WAS} := i_{B_max_AB} = 1.242 \text{ mA}$$

$$A_{CE} = 3$$

$$R_{IN} = (\beta + 1) \cdot (r_e + R_E)$$

$$i_B = \frac{v_{in}}{R_{IN}}$$

$$v_o = -R_C \cdot i_b \cdot \beta$$

$$v_o = -R_C \cdot \frac{v_i}{R_{IN}} \cdot \beta$$

$$\frac{v_o}{v_i} = -\frac{R_C}{(r_e + R_E)} \cdot \frac{\beta}{\beta + 1}$$

$$\frac{v_o}{v_i} = -\alpha \cdot \frac{R_C}{r_e + R_E} = -\alpha \frac{R_C}{R_E} \quad \alpha := \frac{\beta}{\beta + 1} = 0.997$$

$$R_C := 3 \text{ k}\Omega$$

$$A_{CE} = -\alpha \cdot \frac{R_C}{R_E} \quad R_E := \alpha \cdot \frac{R_C}{A_{CE}} = 0.997 \text{ k}\Omega$$

$$R_{E_AC} := 1 \text{ k}\Omega$$

DC

$$V_{CE} := 7.5 \text{ V} \quad I_E := 5 \text{ mA}$$

$$0 \text{ V} = V_{CC} - R_C \cdot I_E \cdot \alpha - R_{E_DC} \cdot I_E - V_{CE} - V_{EE} \quad R_{E_DC} \cdot I_E = V_{CC} - R_C \cdot I_E \cdot \alpha - V_{CE} - V_{EE}$$

$$R_{E_DC} := \frac{V_{CC} - R_C \cdot I_E \cdot \alpha - V_{CE} - V_{EE}}{I_E} = 1.509 \text{ k}\Omega$$

$$R_{E_DC} := 1.5 \text{ k}\Omega$$

$$R_{E_AC} = \frac{R_{E_DC} \cdot R_{E_comp}}{R_{E_DC} + R_{E_comp}} \quad R_{E_comp} := \frac{-(R_{E_DC} \cdot R_{E_AC})}{R_{E_AC} - R_{E_DC}} = 3 \text{ k}\Omega$$

$$V_C := V_{CC} - R_C \cdot I_E \cdot \alpha = 0.046 \text{ V}$$

$$V_E - I_E \cdot R_E - V_{EE} = 0$$

$$V_E := I_E \cdot R_{E_DC} + V_{EE} = -7.5 \text{ V}$$

$$V_B := V_E + V_{BE} = -6.8 \text{ V}$$

DC

$$V_B = \frac{R_{B1} - R_{B2}}{R_{B1} + R_{B2}} \cdot V_{CC} \quad V_{CE} := V_C - V_E = 7.546 \text{ V}$$

$$R_{B1} := 10 \text{ k}\Omega$$

$$V_B = \frac{R_{B1} - R_{B2}}{R_{B1} + R_{B2}} \cdot V_{CC}$$

$$R_{B2} := \frac{R_{B1} \cdot V_{CC} + R_{B1} \cdot V_B}{V_{CC} - V_B} = 3.761 \text{ k}\Omega$$

$$R_{B2} := 3.6 \text{ k}\Omega$$

$$V_B := \frac{R_{B2} - R_{B1}}{R_{B2} + R_{B1}} \cdot V_{CC} = -7.059 \text{ V}$$

$$\frac{15 \text{ V} - (-6.8 \text{ V})}{15.3 \text{ }\mu\text{A}} = 1.425 \text{ M}\Omega$$

$$I_E := \frac{V_E - V_{EE}}{R_{E_DC}} = 5 \text{ mA}$$

$$15 \text{ V} - 15.3 \text{ }\mu\text{A} \cdot 1.5 \text{ M}\Omega = -7.95 \text{ V}$$

$$I_B := \frac{I_E}{(\beta + 1)} = 15.337 \text{ }\mu\text{A}$$

$$S.429$$

Common mode amplifier

DC analyse del 1

$$V_{B_CM} := 0 \text{ V}$$

$$V_{E_CM} := V_{B_CM} - V_{BE} = -0.7 \text{ V}$$

$$V_{CE} := 0.2 \text{ V}$$

Vi antager 0.2V over collector emitter

$$V_{C_CM} := V_{E_CM} + V_{CE} = -0.5 \text{ V}$$

$$I_{EE_CM} := 4 \text{ mA}$$

$$\alpha = 0.997$$

$$I_{E_CM} := \frac{I_{EE_CM}}{2} = 2 \text{ mA}$$

$$\frac{15 \text{ V} - 1.8 \text{ V}}{7.5 \text{ k}\Omega} = 1.76 \text{ mA}$$

$$V_{C_CM} = V_{CC} - R_{C_CM} \cdot I_{E_CM} \cdot \alpha$$

$$V_{BE} = 0.7 \text{ V}$$

$$R_{C_CM} := \frac{V_{CC} - V_{C_CM}}{I_{E_CM} \cdot \alpha} = 7.774 \text{ k}\Omega$$

$$R_{C_CM} := 7.5 \text{ k}\Omega$$

AC diff

$$r_e := \frac{V_T}{I_{E_CM}} = 12.5 \text{ }\Omega$$

$$A_{diff} = 42$$

$$\frac{v_d}{2} = i_b \cdot r_\pi + i_e \cdot R_{E_CM} = i_b \cdot (\beta + 1) \cdot r_e + i_b \cdot (\beta + 1) \cdot R_{E_CM} = i_b \cdot (\beta + 1) (r_e + R_{E_CM})$$

$$v_d = 2 \cdot i_b \cdot (\beta + 1) (r_e + R_{E_CM})$$

$$v_{o1_cm} = -\beta \cdot i_{b_cm} \cdot R_{C_CM}$$

$$A = \frac{X}{2 \cdot (Y + B)}$$

$$\frac{v_{o1_cm}}{v_d} = \frac{-\beta \cdot i_b \cdot R_{C_CM}}{2 \cdot i_b \cdot (\beta + 1) \cdot (r_e + R_{E_CM})} = -\frac{\beta \cdot R_{C_CM}}{2 \cdot (\beta + 1) \cdot (r_e + R_{E_CM})}$$

$$R_{E_CM} := \frac{(- (2 \cdot A_{diff} \cdot r_e) + R_{C_CM}) \cdot \beta - 2 \cdot A_{diff} \cdot r_e}{2 \cdot A_{diff} \cdot \beta + 2 \cdot A_{diff}} = 76.512 \text{ }\Omega$$

$$R_{E_CM} := 75 \text{ }\Omega$$

$$R_{IN} := 2 \cdot (\beta + 1) (r_e + R_{E_CM}) = 57.05 \text{ k}\Omega$$

$$A_{diff} := -\frac{\beta \cdot R_{C_CM}}{2 \cdot (\beta + 1) \cdot (r_e + R_{E_CM})} = -42.726$$

DC del 2

$$0 \text{ V} - V_{BE} - R_{E_CM} \cdot I_{E_CM} - R_{EE_CM} \cdot I_{EE_CM} - V_{CE} - V_{EE} = 0 \text{ V}$$

$$R_{EE_CM} := \frac{V_{BE} - R_{E_CM} \cdot I_{E_CM} - V_{CE} - V_{EE}}{I_{EE_CM}} = 3.838 \text{ k}\Omega$$

$$R_{EE_CM} := 3.9 \text{ k}\Omega$$

AC commen mode

$$v_{CM} = i_b \cdot (\beta + 1) \cdot r_e + (\beta + 1) \cdot R_{E_CM} + 2 \cdot i_b \cdot (\beta + 1) \cdot R_{EE_CM}$$

$$v_{o1_cm} = -\beta \cdot i_{b_cm} \cdot R_{C_CM}$$

$$A_{CM} = \frac{v_{o1_cm}}{v_{CM}} = \frac{-\beta \cdot i_{b_cm} \cdot R_{C_CM}}{i_b \cdot (\beta + 1) \cdot r_e + i_b \cdot (\beta + 1) \cdot R_{E_CM} + 2 \cdot i_b \cdot (\beta + 1) \cdot R_{EE_CM}}$$

$$\frac{-\beta \cdot R_{C_CM}}{(\beta + 1) \cdot r_e + (\beta + 1) \cdot R_{E_CM} + 2 \cdot (\beta + 1) \cdot R_{EE_CM}}$$

$$A_{CM} := \frac{-\beta \cdot R_{C_CM}}{(\beta + 1) \cdot (r_e + R_{E_CM} + 2 \cdot R_{EE_CM})} = -0.948$$

$$CMRR := 20 \cdot \log \left(\frac{A_{diff}}{A_{CM}} \right) = 33.078$$

Strøm spejl

$$I_{C_SP} := I_{EE_CM} = 4 \text{ mA}$$

$$I_{B_SP} := \frac{I_{C_SP}}{\beta} = 12.308 \text{ }\mu\text{A}$$

$$I_{R_SP} := I_{B_SP} \cdot 2 + I_{C_SP} = 4.025 \text{ mA}$$

$$V_{CC} - R_{SP} \cdot I_{R_SP} - V_{BE} - V_{EE} = 0$$

$$R_{SP} := \frac{V_{CC} - V_{EE} + V_{BE}}{I_{R_SP}} = 7.628 \text{ k}\Omega$$